1

IMPLEMENTATION OF SEQUENCE DETECTOR USING LED IN IOT

Marri Srinath Reddy srinathreddymarri@gmail.com IITH - Future Wireless Communication

2

CONTENTS

I Question 1 II **Answer** 1 II-A Truth Table 1 II-B K-Map Implementation of y1 II-C K-Map Implementation of D1 2 II-D K-Map Implementation of D22 Ш **Components** 2

I. QUESTION

A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequence detectable. For the sequence (1,0,1) and input data (1,1,0,1,0,0,1,1,0,1,0,1,1,0)

1) 1,1,0,0,0,0,1,1,0,1,0,0


Implementation

IV

- 2) 0,1,0,0,0,0,0,1,0,1,0,0
- 3) 0,1,0,0,0,0,0,1,0,1,1,0
- 4) 0,1,0,0,0,0,0,1,0,1,0,0

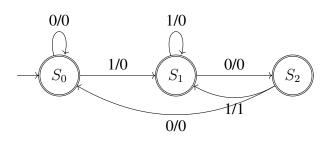II. ANSWER

The above question can be solved by using State diagram, Truth Table and karnaugh-map.



A. Truth Table

p	q	x	\bar{p}	\bar{q}	y	<i>D</i> 1	D2
$\frac{P}{0}$	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	0	0	0	0	0
1	0	1	0	1	1	0	1
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Truth table for Boolean function

B. K-Map Implementation of y

qx00 11 01 10 0 0 0 0 0 p1 1 X X 0

Table. 1 Therefore, the Boolean function is y = px.

C. K-Map Implementation of D1 qx

		00	01	11	10
p	0	0	0	0	1
	1	0	0	X	X

Table. 2 Therefore, the Boolean function is $D1 = q\bar{x}$.

D. K-Map Implementation of D2

qx

00 01 11 10

0 0 1 1 0

1 0 1 X

Table. 3 Therefore, the Boolean function is D2 = x.

III. COMPONENTS

Components	Values	Quantity
Vamanboard		1
Jumper	M-M	7
Wires		
Breadboard		1
LED		2
Resistor	220 ohms	2

IV. IMPLEMENTATION

Vaman PIN	INPUT	OUTPUT
2	manual	
4		LED
13		LED

Procedure

1. Connect the circuit as per the above table.

2. Upload the IOT code from the below link.

https://github.com/SrinathReddyMarri/FWC///blob/master/IOT/main.cpp

3. Change the values of **Inputs** in the Hardware and verify the sequence.