

ARM ASSIGNMENT

Marri Srinath Reddy
 srinathreddymarri@gmail.com
 IITH - Future Wireless Communication

CONTENTS

I Question

II Answer

III Truth Table

IV Logic Diagram

V Components

VI Implementation

II. ANSWER

The above question can be solved by grouping 1's. Therefore the answer is $\bar{R}Q + S$

PQ

		00	01	11	10
00		0	1	1	0
01		1	1	1	1
11	RS	1	1	1	1
10		0	0	0	0

I. QUESTION

The output expression for the karnaugh map shown below is

PQ

		00	01	11	10
00		0	1	1	0
01		1	1	1	1
11	RS	1	1	1	1
10		0	0	0	0

III. TRUTH TABLE

R	S	P	Q	K
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Truth table for Boolean function K

- (A) $\bar{R}Q + S$
- (B) $QR + \bar{S}$
- (C) $QR + S$
- (D) $QR + \bar{S}$

IV. LOGIC DIAGRAM

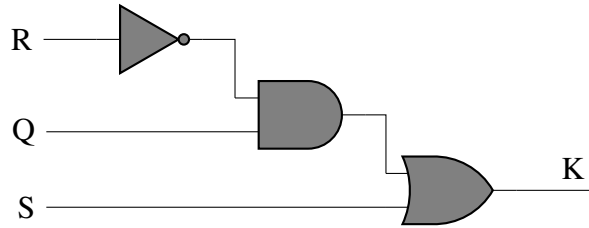


Fig. 2

V. COMPONENTS

Components	Values	Quantity
VAMAN		1
Jumper Wires	M-F	7
Breadboard		1
LED		1
Resistor	100ohms	1

VI. IMPLEMENTATION

VAMAN PIN	INPUT	OUTPUT
23	R	
24	S	
25	P	
22	Q	
21		K

Connections

Procedure

1. Connect the circuit as per the above table.
2. Connect inputs to Vcc for Logic 1, ground for Logic 0.
3. Execute the circuit using the below codes.

<https://github.com/SrinathReddyMarri/FWC/blob/master/ARM/main.c>

4. Change the values of R, S, P, Q in the Hardware and verify the Truth Table.